

# DC circuit analysis

Avinash Chand Yadav

Department of Physics & Astronomical Sciences  
Central University of Jammu  
Samba 181 143, India.

*jnu.avinash@gmail.com*

May 22, 2017

## RC circuit

- Consider a  $RC$  series circuit with resistor  $R$  and capacitor  $C$  connected with a constant voltage source  $V$ .

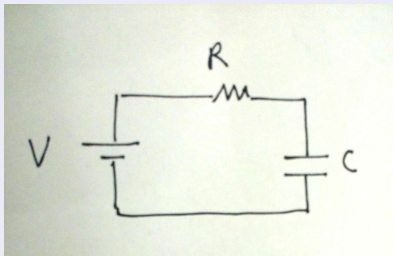


Figure 1: A typical  $RC$  series circuit.

## Analysis

- Using Kirchoff's voltage law, we write

$$V = V_R + V_C,$$

$$V = RI + q/C,$$

$$V = R \frac{dq}{dt} + \frac{q}{C}. \quad (1)$$

- Rearranging, we can write

$$\frac{dq}{dt} + \frac{q}{\tau} = \frac{V}{R}, \quad (2)$$

where  $\tau = RC$  is the characteristic time constant.

- This is a first order linear ordinary differential equation.

...

- Solving the Eq. (2), we find charge as a function of time

$$q(t) = CV[1 - \exp(-t/\tau)]. \quad (3)$$

- The corresponding current decreases exponentially as

$$I(t) = \frac{dq}{dt} = \frac{V}{R} \exp(-t/\tau). \quad (4)$$

- The voltage across capacitor increases as

$$V_C = \frac{q}{C} = V[1 - \exp(-t/\tau)]. \quad (5)$$

## RL circuit

- Consider a  $RL$  series circuit with resistor  $R$  and inductor  $L$  connected with a constant voltage source  $V$ . A similar analysis can be done here.
- The current as a function of time increases as

$$I(t) = \frac{V}{R}[1 - \exp(-t/\tau)], \quad (6)$$

where  $\tau = L/R$ .

- The voltage across inductor decreases as

$$V_L = V \exp(-t/\tau). \quad (7)$$